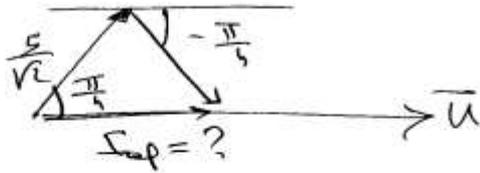


II



④

$$\vec{I}_{\phi} = \vec{I}_{\phi 1} + \vec{I}_{\phi 2}$$

$$I_{\phi}^2 = \left(\frac{5}{\sqrt{2}}\right)^2 + \left(\frac{5}{\sqrt{2}}\right)^2$$

$$I_{\phi} = 5A$$

في طرف الوترين ⑤

بعد  
من طرف الـ C

$$\sqrt{(R+R')^2 + X_L^2} = \sqrt{R^2 + (X_L - X_C)^2}$$

$$X_L^2 = (X_L - X_C)^2$$

$$X_L = X_L - X_C \Rightarrow X_C = 0$$

$C \rightarrow \infty$   
رقعة

$$X_L = -(X_L - X_C) \Rightarrow X_C = 2X_L$$

من

$$40\sqrt{2} = \sqrt{(40)^2 + X_L^2}$$

$$X_L = 40 \Omega$$

$$X_C = 80 \Omega$$

$$C = \frac{1}{8000\pi} F$$


سبب  $I_{\phi}$  الجيب في الزاوية



$$\phi_2 = +\frac{\pi}{4}$$

$X_C > X_L$
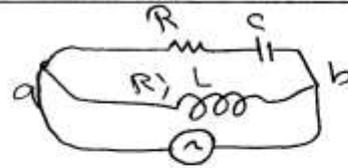
$$I_{\phi} = \frac{5}{\sqrt{2}} + \frac{5}{\sqrt{2}} = \frac{10}{\sqrt{2}} A$$



أولاً

فرع 1:  $R = 40 \Omega, C = \frac{1}{4000\pi} F$

فرع 2:  $R' = 40 \Omega, \text{Cond} = \frac{1}{12} \mu F$

①  $Z = 40 \Omega$

$$Z_1 = \sqrt{R^2 + X_C^2}$$

$$X_C = \frac{1}{\omega C} = \frac{1}{100\pi \frac{1}{4000\pi}} = 40 \Omega$$

$$Z_1 = \sqrt{(40)^2 + (40)^2} = 40\sqrt{2} \Omega$$

$$Z_2 = \sqrt{R'^2 + X_L^2}, \text{Cond} = \frac{R'}{Z_2}$$

$$Z_2 = \frac{R'}{\text{Cond}} = 40\sqrt{2} \Omega$$

$$I_{\phi 1} = \frac{U_{\phi 1}}{Z_1} = \frac{200}{40\sqrt{2}} = \frac{5}{\sqrt{2}} A \quad \text{②}$$

$$I_{\phi 2} = \frac{U_{\phi 2}}{Z_2} = \frac{200}{40\sqrt{2}} = \frac{5}{\sqrt{2}} A$$

$$i = I_{\max} \cos(100\pi t + \phi)$$

$$i_1 = \frac{5}{\sqrt{2}} \cos(100\pi t + \frac{\pi}{4})$$

$$\left( \begin{aligned} \text{Cond}_1 &= \frac{R}{Z_1} = \frac{40}{40\sqrt{2}} = \frac{1}{\sqrt{2}} \\ \phi_1 &= \frac{\pi}{4} \text{ rad} \end{aligned} \right)$$

$$i_2 = \frac{5}{\sqrt{2}} \cos(100\pi t - \frac{\pi}{4})$$

$$P_{\text{av}1} = U_{\phi 1} \cdot I_{\phi 1} \cdot \text{Cond}_1 = 200 \cdot \frac{5}{\sqrt{2}} \cdot \frac{1}{\sqrt{2}} = 500 \text{ Wat} \quad \text{③}$$

$$P_{\text{av}2} = 500 \text{ Wat}$$

∴  $P_{\text{av}} = 1000 \text{ W}$

2

أولاً

$$Q_1 = S_1 v_1 = S_2 v_2$$

$$\pi r_1^2 v_1 = \pi r_2^2 v_2$$

$$(5 \times 10^{-2})^2 \cdot 4 = (10 \times 10^{-2})^2 v_2 \Rightarrow v_2 = 1 \text{ ms}^{-1}$$

$$Q_1 = S_1 v_1 = \pi \cdot 25 \times 10^{-4} \cdot 4$$

$$= \pi \times 10^2 \text{ m}^3 \text{ s}^{-1}$$

$$Q = \rho Q_1 = 1000 \cdot \pi \cdot 10^{-2}$$

$$= 10\pi \text{ kg s}^{-1}$$

$$P_1 - P_2 = \frac{1}{2} \rho (v_2^2 - v_1^2) + \rho g (z_2 - z_1)$$

$$= \frac{1}{2} 10^3 (1 - 16) + 5000$$

$$= -2.5 \times 10^3 \text{ Pa}$$

$$W = \Delta E_K + \Delta E_P \quad (3)$$

$$\frac{W}{V} = \frac{\Delta E_K}{V} + \frac{\Delta E_P}{V}$$

$$= \frac{1}{2} \rho (v_2^2 - v_1^2) + \rho g (z_2 - z_1)$$

$$= P_1 - P_2 = -2.5 \times 10^3$$

$$W = -2.5 \times 10^3 \times 10^{-1}$$

$$= -2.5 \times 10^2 \text{ J}$$

$$P_1 - P_2 = \rho g (z_2 - z_1) \quad (4)$$

$$= 10^3 \cdot 10 \cdot \frac{1}{2} = 5 \times 10^3 \text{ Pa}$$

( $v_1 = v_2 = 0$  :  $\frac{1}{2} \rho v^2$ )

ثانياً

بما أن  $d = 0$  مع  $i$  و  $u$  في  
الدار في حالة تيارات مترابطة

$$Z = R$$

$$Z = \frac{U_{\text{eff}}}{I_{\text{eff}}} = \frac{100}{5} = 20 \Omega$$

$$R = 20 \Omega$$

$$X_L = X_C \Rightarrow \frac{1}{\pi} \cdot 100 \pi = \frac{1}{100 \pi C}$$

$$C = \frac{1}{10000 \pi} \text{ F}$$

$$P_{\text{av}} = R I_{\text{eff}}^2 \quad (2)$$

$$= 20 (5)^2 = 500 \text{ W}$$


(طاقة)

$$(3) U_{\text{eff}L} = X_L I_{\text{eff}} = 100 \cdot 5 = 500 \text{ V}$$

$$u = U_{\text{max}} \cos(100 \pi t + \varphi)$$

$$U_{\text{eff}} = X_L I_{\text{eff}} = 100 \cdot 5 = 500 \text{ V}$$
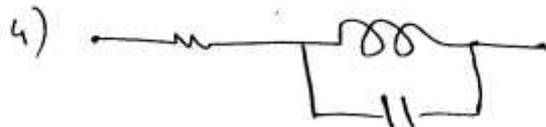
$$u = 500\sqrt{2} \cos(100 \pi t + \frac{\pi}{2})$$



$$I_{\text{eff}L} = \frac{U_{\text{eff}}}{X_L}$$

$$I_{\text{eff}C} = \frac{U_{\text{eff}}}{X_C}$$

$$X_L = X_C \Rightarrow I_{\text{eff}L} = I_{\text{eff}C}$$

$$\vec{I}_{\text{eff}} = \vec{I}_{\text{eff}L} + \vec{I}_{\text{eff}C}$$

$I_{\text{eff}L} = I_{\text{eff}C}$   
اضدادان

3

المعروف:  $\lambda = 1 \text{ m}$   
 $m = 10^{-2} \text{ Kg}$   
 $f = 50 \text{ Hz}, F_T = 4 \text{ N}$

$$\mu = \frac{m}{\lambda} = \frac{10^{-2}}{1} = 10^{-2} \text{ Kg m}^{-1} \quad (1)$$

$$v = \sqrt{\frac{F_T}{\mu}} = \sqrt{\frac{4}{10^{-2}}} = 20 \text{ ms}^{-1}$$

$$v = \lambda f \Rightarrow \lambda = \frac{20}{50} = 0,4 \text{ m}$$

$$\text{عدد الأطوال الموجبة} = \frac{\lambda}{\lambda} = \frac{1}{0,4} = 2,5 \quad (2)$$

(3)

$$y_{\text{max/n}} = 2y_{\text{max}} \left| \sin^2 \frac{\pi}{\lambda} z \right|$$

$$= 2 \cdot 1 \times 10^{-2} \sin^2 \frac{2\pi}{0,4} \cdot 0,2$$

$$= 0 \quad (\text{عقدة})$$

$$\mu = \rho S \quad (3)$$

$$\rho = \frac{10^{-2}}{10^{-5}} = 10^3 \text{ Kg m}^{-3}$$

$$v_{\text{max}} = \omega_c y_{\text{max}} \quad (4)$$

$$= 2\pi \cdot 50 (2 \times 1 \times 10^{-2})$$

$$= 4\pi \text{ ms}^{-1}$$

$$K \sqrt{F_T} = K' \sqrt{F_T'} \quad (5)$$

$$K = 25 \times 2 = 5 \text{ صفائح}$$

$$5 \sqrt{4} = 1 \sqrt{F_T'}$$

$$F_T' = 100 \text{ N}$$


مناقشة: مسأله / مكانيك سائل:

$$W = +600 \text{ J}$$

$$P_1 - P_2 = \frac{1}{2} \rho (v_2^2 - v_1^2) \quad (3)$$

$$= \frac{1}{2} \times 10^3 (16 - 4)$$

$$= +6000 \text{ Pa}$$

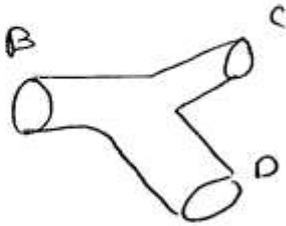

$$Q_c = \frac{1}{9} Q_B$$

$$Q_B = Q_c + Q_D$$

$$= Q_c + 9 Q_c$$

$$Q_B = 10 Q_c$$

$$8 \times 10^{-2} = 10 Q_c \Rightarrow Q_c = 8 \times 10^{-3}$$

$$Q_c = S_c \cdot v_c \Rightarrow v_c = \frac{8 \times 10^{-3}}{10^{-2}} = 0,8 \text{ ms}^{-1}$$

$$Q_c = \frac{1}{9} S_D v_D$$

$$8 \times 10^{-3} = \frac{1}{9} \times S_D \cdot 3$$

$$S_D = 24 \times 10^{-3} \text{ m}^2$$

$$Q = S_1 v_1 = 10 \times 10^{-2} \cdot 20 \quad (5)$$

$$Q = 2 \times 10^{-2} \text{ m}^3 \text{ s}^{-1}$$

$$Q = S_2 v_2 \Rightarrow v_2 = \frac{1}{2} v_1 = 10 \text{ ms}^{-1}$$

$$P_1 + \frac{1}{2} \rho v_1^2 + \rho g z_1 = P_2 + \frac{1}{2} \rho v_2^2 + \rho g z_2$$

$$z_1 - z_2 = h = 1 \text{ m}$$

$$10^5 + \frac{1}{2} \times 10^3 \cdot 400 + 1000 \cdot 10 \cdot (10) = P_2 + \frac{1}{2} \times 10^3 \cdot 100$$

$$P_2 = 350 \times 10^3 \text{ Pa}$$

$$B = W - W' \quad (1)$$

$$W' = 5,4 - 2,7 = 2,7 \text{ N} \quad (2)$$

$$B = \rho g V \quad (3)$$

$$V = \frac{2,7}{10^3 \cdot 10} = 2,7 \times 10^{-4} \text{ m}^3$$

$$W = \rho g V' \quad (5)$$

$$V' = \frac{5,4}{2700 \cdot 10} = 2 \times 10^{-4} \text{ m}^3$$

$$V'' = 2,7 \times 10^{-4} - 2 \times 10^{-4} = 0,7 \times 10^{-4} \text{ m}^3$$

$$B = \rho g V \quad (4)$$

$$2,16 = \rho \cdot 10 \cdot 2,7 \times 10^{-4}$$

$$\rho = 800 \text{ kg m}^{-3}$$

$$V = 2,7 \times 10^{-4} \text{ m}^3 \quad (5)$$

$$Q = 0,08 \text{ m}^3 \text{ s}^{-1} \quad (2)$$



$$S_A = 0,04 \text{ m}^2$$

$$v_B = 4 \text{ ms}^{-1}$$

$$Q = S_A v_A \quad (1)$$

$$v_A = \frac{8 \times 10^{-2}}{4 \times 10^{-2}} = 2 \text{ ms}^{-1}$$

$$S_B = \frac{8 \times 10^{-2}}{4} = 2 \times 10^{-2} \text{ m}^2$$

$$W = \Delta E_K \quad (2)$$

$$\frac{W}{V} = \frac{\Delta E_K}{V} = \frac{1}{2} \rho (v_2^2 - v_1^2)$$

$$\frac{W}{0,1} = \frac{1}{2} \times 10^3 (16 - 4) = 5000 \text{ J}$$